Practice Question Set For A-Level

**Subject : Physics** 


Paper-1 Topic: Electricity



Name of	the Student:	
Max. Ma	rks : 24 Marks	Time: 24 Minutes
Q1.		
	dioactive source emits alpha particles each with 8.1 $\times$ 10 <sup>-13</sup> J of kinetic energy.	
(a)	Show that the velocity of an alpha particle with kinetic energy 8.1 $\times$ 10 <sup>-13</sup> J is app 10 <sup>7</sup> m s <sup>-1</sup>	roximately 2 ×
	specific charge of an alpha particle = $4.81 \times 10^7 \text{ C kg}^{-1}$	
		(2)
(b)	The alpha particles travel through air in straight lines with a range of 3.5 cm	(-/
	Calculate the average force exerted on an alpha particle as it is stopped by the	air.
	average force =	N <b>(2)</b>
(c)	An alpha particle transfers all its kinetic energy to air molecules and produces 5 per centimetre over its range of 3.5 cm	

Calculate the average ionisation energy, in eV, of a molecule of air.

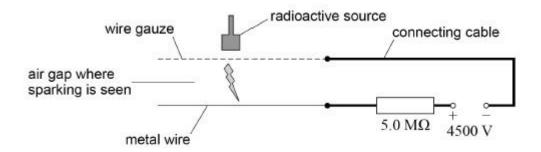(d) A spark counter consists of a wire gauze separated from a metal wire by a small air gap. A power supply with an output of 4500 V is connected in series with a 5.0 M $\Omega$  resistor and the spark counter as shown in the diagram. When the radioactive source is moved close to the wire gauze, sparking is seen in the air gap.



Sparks are produced when alpha particles produce ionisation in the air gap.

One ionisation event produces a current of 0.85 mA for a time of 1.2 ns

Calculate the number of charge carriers that pass a point in the connecting cable during this ionisation event.

	number of charge carriers =	
		(2)
(e)	The radioactive source was positioned 10 cm above the wire gauze before being moved slowly towards the wire gauze leading to the ionisation event in part <b>(d)</b> .	

Discuss how the potential difference across the air gap varied as the radioactive source was

Assume the power supply has negligible internal resistance.


moved over this distance.

(3)

(Total 12 marks)

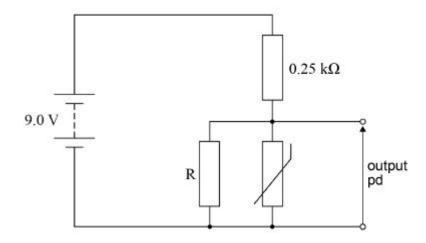**Q2**.

The diagram shows a circuit designed by a student to monitor temperature changes.



The supply has negligible internal resistance and the thermistor has a resistance of 750  $\Omega$  at room temperature. The student wants the output potential difference (pd) at room temperature to be 5.0 V

(a) The 0.25 k $\Omega$  resistor is made of 50 turns of wire that is wound around a non-conducting cylinder of diameter 8.0 mm

Resistivity of the wire =  $4.2 \times 10^{-7} \Omega \text{ m}$ 

Determine the area of cross-section of the wire that has been used for the resistor.

area of cross-section = 
$$_{ } m^2$$
 (3)

(b) The student selects a resistor rated at 0.36 W for the 0.25 k $\Omega$  resistor in the diagram.

Determine whether this resistor is suitable.

etermine the value of R that the	ne student sho	uld select.		
sive your answer to an approp	riate number o	f significant figure	<del>9</del> S.	
		value of R =		Ω
tate and explain the effect on	the output pd o	of increasing the	temperature of the t	thermistor
				_
				_