

Name of the Student: \_\_\_\_\_

Max. Marks : 24 Marks

Time : 24 Minutes

## Mark Schemes

## Q1.

- (a) (i)  $230 \times \sqrt{2} = 325 \text{ (V)}$  ✓  
 $(2 \times 325 =) 650 \text{ to } 651 \text{ V}$  ✓

*allow doubling their incorrect peak voltage ( $162.6 \times 2$ ) by use of  $\sqrt{2}$  as an attempt to find peak-to-peak for 1 mark but not just  $2 \times 230$*

2

- (ii) (use of  $P = V^2/R$ )

$$P = 230^2/12 \text{ ✓}$$

$$P = 4.4 \times 10^3 \text{ (W)} \text{ ✓ } \text{cao}$$

2 sig. figs. Incorrect answer must be supported by working ✓

*Allow their incorrect answer  $(a)(i)^2 \div 12$*

**Or**  $325^2 \div 12$  as a use of for 1 mark

*Alternative*

*For first mark*

$$I = \frac{V}{R} \text{ and } P=VI \text{ allowing their incorrect answer}$$

*(a)(i) or 325 as sub for V for 1 mark*

*Answers 8.8 kW (325V) and 35 kW (650V)*

3

- (b) (i) there is a pd / voltage across the cable ✓  
 pd / voltage across cooker is 230 V minus this pd / voltage ✓  
 2nd mark depends on 1st mark in all

*The current is lower due to the resistance of cable / The current is lower as circuit resistance increases ✓*

*pd across oven is lower since  $V=I \times \text{Resistance of element}$  ✓*

**or**

*Resistance of the cable is in series with element ✓*

*Voltage splits (in ratio ) across these resistances ✓*

2

- (ii) resistance of cable =  $2 \times 3.15 \times 0.0150 = 0.0945$  ✓

*Allow power 10 error here*

$$V = \frac{12}{12 + R_{\text{cable}}} \times 230 \text{ ✓}$$

$$\text{Or } I = \frac{230}{12 + R_{\text{cable}}} \text{ and } V = \left( \frac{230}{12 + R_{\text{cable}}} \right) \times 12$$

=228 V ✓ cao

*Allow their incorrect  $R_{\text{cable}}$  correctly substituted for 2nd marking*

3

- (iii) 230 – their (b) (ii) or 19 (A) quoted for current or equivalent seen in equation (230 / 12.0945) ✓

( $P =$ ) 34.2 to 42.3(W) ✓ correct working

ecf as  $P = (230 - (b)(ii))^2 / \text{their } R_{\text{cable}}$

2

- (iv) minimise power loss / maximise efficiency of oven / ensure element gets as hot as possible ✓

avoid overheating / fires ✓

*not just to carry a large current / larger pd across element*

*Either order*

2

[14]

## Q2.

- (a) time base is (switched) off ✓  
TO for y-input switched off

*not affected by x plates because these plates are not switched on*

1

- (b) (i) emf (of battery) ✓

*not just terminal pd*

*TO applied for non-emf statements*

*Allow explanation of emf*

1

- (ii) (emf =  $3 \times 2.0 =$ ) 6.0 V ✓

*penalise 1 sf*

1

- (c) Because the pd across the y plates has decreased ✓

there is a current (in the battery) ✓

there is a pd / voltage across the internal resistance **or** there are (now) lost volts ✓

terminal pd decreases **or** terminal pd now less than emf **or**  $IR = \varepsilon - Ir$  ✓

3

- (d)  $V = 2.5 \times 2.0 = 5$  V

**or** (use of  $V = IR$ ) by  $I =$  their incorrect voltage  $\div 18$  ✓

*Must see  $I$  as subject or their working leading to answer line for use of*

$I = 0.28$ (A) ✓ cao

2

- (e) (use of  $\varepsilon = IR + Ir$ )

$6.0 = 2.5 \times 2.0 + 0.28 \times r$

$$r = \frac{\varepsilon - IR}{I}$$

or correct rearrangement to make  $r$  subject

or sets  $R_{(r)} = \frac{\varepsilon}{0.28} = 21.2$  or  $21.4$  (ohms) with subject seen

or  $\frac{1}{0.28}$  ✓

$r = 3.4$  to  $3.6 \Omega$  ✓

*Ecf for  $I$  and  $V$*  ecf ans =  $\frac{6 - \text{their } V}{\text{their } I}$

2

[10]