

Name of the Student: \_\_\_\_\_

Max. Marks : 21 Marks

Time : 21 Minutes

Mark Schemes

**Q1.**

- (a) (Dielectric constant is)  $\frac{\text{permittivity of medium}}{\text{permittivity of free space}}$  and is equal to 6 ✓  
 OR

The permittivity of the dielectric is 6 times the permittivity of free space

Allow:  $\frac{C \text{ with dielectric (between plates)}}{C \text{ in a vacuum}} = 6.$

*Its not enough to quote relative permittivity = 6*

1

- (b) (Electric field exists between plates)

Polar molecules align with their positive side facing the negative plate (owtte) ✓<sub>1</sub>

✓<sub>1</sub> or vice versa.

producing a counter electric field/reducing the field between the plates ✓<sub>2</sub>

The pd  $V$  reduces between the capacitor plates but charge  $Q$  remains the same so capacitance  $Q/V$  increases. ✓<sub>3</sub>

✓<sub>3</sub> This mark may be approached from the idea that more charge would be required to maintain pd hence  $C$  increases by referencing  $C = Q/V$

3

- (c)  $Q$  remains the same ✓<sub>1</sub>

New  $C$  is 6 x previous  $C$  ✓<sub>2</sub>

✓<sub>2</sub> May be seen in the substitution in the energy difference calculation

Energy difference =  $3.8 \times 10^{-9} \text{ J}$  ✓<sub>3</sub>

✓<sub>3</sub> Calculates change in energy using  $E = \frac{1}{2}Q^2\left(\frac{1}{c_2} - \frac{1}{c_1}\right) = 4.58 \times 10^{-9} - 7.64 \times 10^{-10}$

Where  $Q = 7.6 \times 10^{-10} \text{ C}$  :  $c_1 = 63 \times 10^{-12} \text{ F}$

and  $c_2 = 6 \times 63 \times 10^{-12} \text{ F}$   $E = 378 \times 10^{-12} \text{ J}$


Condone a negative final answer

If no marks given award single mark for the initial energy stored =  $4.58 \times 10^{-9} \text{ J}$

3

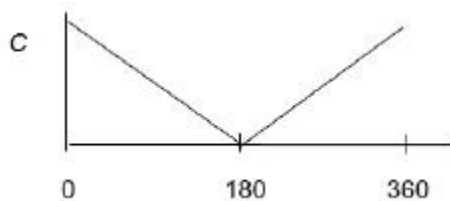- (d) showing a linear decrease and increase ✓

points correct at 0, 180 and 360 degrees ✓



Ignore graph beyond 360 degrees

2

- (e) Insert dielectric between plates/attach dielectric to one plate  
OR reduce air gap explained ✓

Dielectric has  $\epsilon_r = 4$  ✓

air gap reduced to  $\frac{1}{4}$  ✓

1st mark for quantitative answer for air gap or dielectric or both.

(Allow: more plates when explained)

2nd and 3rd marks for numerical analysis for air gap **and** dielectric change. Do not allow incorrect physics.

3

[12]

## Q2.

- (a)  $V_{\text{rms}} \left( = \frac{V_{\text{peak}}}{\sqrt{2}} = \frac{15}{\sqrt{2}} \right) = 10.6 \text{ (V)} \checkmark$

{allow 11 V to 2 sig figs}

1

- (b) (Peak voltage 3 divisions corresponding to 15 V)

y-voltage gain =  $5 \text{ (V div}^{-1}\text{)} \checkmark$

1

- (c) A horizontal line drawn at 10.6 V ✓

Tolerance – must be between 10 and 11 up from the centre

Allow ecf from (a)

1

- (d) (Period  $T$  = corresponds to 8 divisions

$$T = 8 \times 5.0 \times 10^{-4} \text{ s} = 0.0040 \text{ s}$$

$$\text{Frequency} = 1/T = 1/0.0040 = 250 \text{ (Hz)} \checkmark$$

Answer only gains the mark.

1

- (e) Time constant =  $4 \times 10^{-4} \text{ (s)} \checkmark_1$  {only needs 1 sig fig}

The second and third mark can come from the following alternatives.

Note the mark is for the method so allow arithmetic slips and imprecise measurements.

To use a number of small divisions rather than grid divisions is not an arithmetic error. This error comes from not knowing how the oscilloscope is used.

Full marks can be awarded from consideration of the charging part of the cycle.

The equation can be presented in a number of variations using  $RC$  or  $\tau$  for example.

$$V_t = V_o e^{-\frac{t}{\text{time constant}}} \quad \checkmark_{2a}$$

Make use of the equation

Substitute values for  $V_t$  and  $V_o$  (confirmed by the graph) and calculate the (unknown) time constant.  $\checkmark_{3a}$

Typical calculation might be:

$$\frac{V_t}{V_o} = \frac{1}{12} \text{ in 2 time divisions. Substitution into the equation will give } \tau$$

$V_t$  and  $V_o$  both need to be defined in relation to the graph

OR

$$\ln 2 (= 0.69) = \frac{\frac{t_1}{2}}{\text{time constant}} \quad \checkmark_{2b}$$

Substitute time for  $V$  to decrease to half its value (confirmed by the graph) and calculate the time constant  $\checkmark_{3b}$

OR

$V$  halves its value in 0.5 time divisions.

Substituting gives  $\tau$

$$\frac{t_1}{2} \text{ needs to be defined in relation to the graph}$$

OR

The voltage falls to  $1/e$  or 37% in a time constant  $\checkmark_{2c}$  {owtte}

Find the time that corresponds to this fall in voltage confirmed by the graph (normally the start of the discharge This gives the  $\tau$  directly)  $\checkmark_{3c}$

OR

37% of 3 divisions is 1.1 divisions which occurs in time  $\frac{3}{4}$  time divisions giving  $\tau$

3

(f) Reduce the time-base setting  $\checkmark_{1a}$

Uncertainty is due to the smallness of the divisions and this action means the waveform/trace stretched horizontally/in x-direction.  $\checkmark_{2a}$  {owtte}

OR

Increase the y-gain  $\checkmark_{1b}$

Uncertainty is due to the smallness of the divisions and this action means the waveform/trace stretched vertically/in y-direction. (The trace will need to be moved vertically to fit on the screen)  $\checkmark_{2b}$  {owtte}

<sub>1</sub> Stated answer must be a practicable change

<sub>2</sub> Explanation must refer to both the trace and its relation to uncertainty and follow a correct change.

2

[9]