

Name of the Student: _____


Max. Marks : 21 Marks

Time : 21 Minutes

Mark Schemes

Q1.

(a) (i)

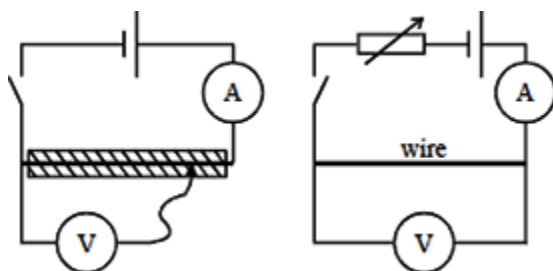

(1) battery, wire, (variable resistor) and ammeter in series

(1) voltmeter connected across wire

- (ii) (α) (with switch closed) measure I and V (1)
 move contact along the wire (1) (or length of wire changed)
 measure new (I and) V (1)
 measure l each time (1)

or (β) measure I and V (1)
 change variable resistor (1)
 measure new I and V (1)
 l known (1)

(iii) $R = \frac{\rho l}{A}$ or $\rho = \frac{RA}{l}$ or $\rho = \frac{A}{l} \times \frac{V}{I}$ (1)

(α) obtain gradient of graph of V or R vs l (1)
 A (and I) known, hence ρ (1)

or (β) gradient of graph of V vs I (1)
 A and l known, hence ρ (1)

[or, for both methods, measure $R = \frac{V}{I}$ for each length (1)

take mean and hence ρ (1)

9

(b) (use of $V = IR$ gives) $R = \frac{240}{2 \times 10^{-3}}$ (1) ($= 120 \times 10^3 (\Omega)$)

$$\rho = \left(\frac{RA}{l} \right) = \frac{120 \times 10^3 \times 80 \times 80 \times 10^{-6}}{1.6 \times 10^{-3}} \quad (1)$$

$$\begin{aligned} & \text{(allow C.E. for value of } R) \\ & = 5.1 \times 10^5 \, \Omega \, \text{m} \quad (1) \end{aligned}$$

3

- (c) four resistors in series (1)

$$R = 4 \times (120 \times 10^3) = 4.8 \times 10^5 \, \Omega \quad (1)$$

(allow C.E. for value of R)

2

[14]

Q2.

- (a) (i) length of card
[or distance travelled by trolley A] (1)
time at which first light gate is obscured
[or time taken to travel the distance] (1)

- (ii) time at which second light gate is obscured
[or distance travelled after collision and time taken] (1)

3

- (b) momentum = mass \times velocity (1)
mass of each trolley (1)
(check whether) $p_{\text{initial}} = p_{\text{final}}$ (1)

max 2

- (c) incline the ramps (1)
until component of weight balances friction (1)
[or identify where the friction occurs (1)
sensible method of reducing (1)]

2

[7]