

Practice Question Set For A-Level  
**Subject : Physics**  
**Paper-1 Topic : 7\_ Electric Field1**

Name of the Student: \_\_\_\_\_

Max. Marks : 17 Marks

Time : 17 Minutes

Mark Schemes


Q1.

Question Number	Acceptable Answer	Additional Guidance	Mark
(i)	<ul style="list-style-type: none"> <li>Bottom plate marked positive</li> <li>Or bottom terminal of power supply marked positive (1)</li> </ul>	Accept top plate marked negative or top terminal of power supply marked negative	1
(ii)	<ul style="list-style-type: none"> <li>Calculates volume of oil drop (1)</li> <li>Use of <math>\rho = \frac{m}{V}</math> (1)</li> <li>Use of <math>E = \frac{V}{d}</math> (1)</li> <li>Use of <math>F = mg</math> and <math>F = Eq</math> (1)</li> <li>Use of <math>N = \frac{q}{e}</math> (1)</li> <li><math>N = 4.2</math> so student's expectation not supported by data</li> <li>Or <math>N = 4.2</math> which is not a whole number (1)</li> <li>Or <math>N = 4.2</math> so taking experimental error into account student's expectation may be supported by data</li> </ul>	<p><u>Example of calculation</u></p> $V = \frac{4}{3} \pi \times (1.78 \times 10^{-6} \text{ m})^3 = 2.36 \times 10^{-17} \text{ m}^3$ $m = 2.36 \times 10^{-17} \text{ m}^3 \times 920 \text{ kg m}^{-3} = 2.17 \times 10^{-14} \text{ kg}$ $E = \frac{4870 \text{ V}}{1.55 \times 10^{-2} \text{ m}} = 3.14 \times 10^5 \text{ V m}^{-1}$ $q = \frac{2.17 \times 10^{-14} \text{ kg} \times 9.81 \text{ N kg}^{-1}}{3.14 \times 10^5 \text{ N C}^{-1}} = 6.78 \times 10^{-19} \text{ C}$ $N = \frac{6.78 \times 10^{-19} \text{ C}}{1.60 \times 10^{-19} \text{ C}} = 4.23$	6

Q2.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<ul style="list-style-type: none"> <li>A pair of corresponding <math>V</math> and <math>t</math> values read from graph (1)</li> <li>Use of <math>V = V_0 e^{-\frac{t}{RC}}</math> Or Use of time constant = <math>RC</math> (1)</li> <li><math>C = 270 \mu\text{F}</math> (1)</li> <li>Use of <math>\pm 20\%</math> with <math>220 \mu\text{F}</math> [Largest <math>C = 264 \mu\text{F}</math>, smallest <math>C = 176 (\mu\text{F})</math>] (1)</li> <li>Comparison of <math>264 (\mu\text{F})</math> [<math>176 (\mu\text{F})</math> if their calculated <math>C</math> is too low] with calculated value of <math>C</math> from graph and conclusion consistent with this (1)</li> </ul>	<p>Allow use of tangent at <math>t = 0</math> to determine intercept on <math>x</math>-axis and obtain value for time constant; then calculate <math>C</math> gives MP1, MP2 and MP3</p> <p>MP3: Value should be correct and have units</p> <p><u>Example of calculation</u></p> $1.0 = 6.0 e^{-\frac{40 \text{ s}}{82 \times 10^3 \Omega \times C}}$ $\therefore \ln\left(\frac{1.0 \text{ V}}{6.0 \text{ V}}\right) = -\frac{40 \text{ s}}{82 \times 10^3 \Omega \times C}$ $\therefore C = \frac{-40 \text{ s}}{-1.79 \times 82 \times 10^3 \Omega} = 2.72 \times 10^{-4} \text{ C}$ <p>Largest value of capacitance = <math>1.2 \times 220 \mu\text{F} = 264 \mu\text{F}</math></p>	5

Q3.

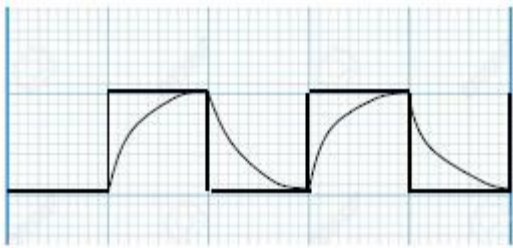Question Number	Acceptable answers	Additional guidance	Mark
	<ul style="list-style-type: none"> <li>Time axis: one cycle = 50 OR two cycles = 100</li> <li>Use of time constant = <math>RC</math></li> <li>Charging curve, from 25 ms to 50 ms, just about reaching 5V as shown (ecf from their T)</li> <li>One corresponding discharge curve</li> <li>Curve should look exponential</li> </ul>	<p>(1)</p> <p><u>Example of calculation</u></p> <p><math>T = 1/f = 1/20 \text{ Hz} = 0.050 \text{ s}</math></p> <p>Two cycles = <math>2 \times 0.050 \text{ s} = 0.10 \text{ s} = 100 \text{ ms}</math></p> <p>Time Constant = <math>100 \times 50 \times 10^{-6} = 0.005 \text{ s}</math></p> <p>In half a cycle (0.025 s) there are <math>0.025 \text{ s} / 0.005 \text{ s} = 5</math> Time constants</p> <p>(1)</p> <p>Ignore anything drawn in the first half cycle</p>  <p>(1)</p> <p>(1)</p> <p>Time period should be marked 50 ms or equivalent</p>	5