

Name of the Student: _____

Max. Marks : 25 Marks

Time : 25 Minutes

Mark Schemes

Q1.

- (a) water heated by radiation (from the Sun)
accept IR / energy for radiation 1

water used to heat buildings / provide hot water
allow for 1 mark heat from the Sun heats water if no other marks given
references to photovoltaic cells / electricity scores 0 marks 1

- (b) 2 (minutes)
- $$1.4 \times 10^3 = \frac{168 \times 10^3}{t}$$
- gains 1 mark*
calculation of time of 120 (seconds) scores 2 marks 3

- (c) (i) 150 (kWh) 1

- (ii) £60(.00) or 6000 (p)
an answer of £6000 gains 1 mark
allow 1 mark for $150 \times 0.4(0)$ 150×40
allow ecf from (c)(i) 2

- (iii) 25 (years)
an answer of $6000 / 240$
or
 $6000 / \text{their (c)(ii)} \times 4$
gains 2 marks
an answer of $6000 / 60$
or
 $6000 / \text{their (c)(ii)}$ gains 1 mark, ignore any other multiplier of (c)(ii) 3

- (iv) any **one** from:
- will get £240 per year
accept value consistent with calculated value in (c)(iii)
 - amount of light is constant throughout the year
 - price per unit stays the same
 - condition of cells does not deteriorate

(d) any **one** from:

- angle of tilt of cells
- cloud cover
- season / shade by trees
- amount of dirt

1

[13]

Q2.

(a) (i) symbol for a diode




accept



1

symbol for a variable resistor

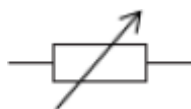

1

(ii) voltmeter is in series **or** voltmeter is not in parallel

1

ammeter is in parallel **or** ammeter is not in series

accept an answer in terms of how the circuit should be corrected
voltmeter and ammeter are wrong way around is insufficient

1

(b) (i) 0.2 (V)

accept any value between 0.20 and 0.21 inclusive

1

(ii) 37.5

allow 1 mark for $I = 0.008$

or

allow 2 marks for correct substitution, ie $0.3 = 0.008 \times R$

or

*allow 1 mark for a correct substitution using $I = 0.8$ **or** $I = 0.08$*

or $I = 0.009$

or

*allow 2 marks for answers of 0.375 **or** 3.75 **or** 33(.3)*

3

(c) (i) 25

allow 1 mark for obtaining period = 0.04(s)

2

(ii) diode has large resistance in reverse / one direction

1

so stops current flow in that / one direction

allow diodes only let current flow one way / direction

allow 1 mark for the diode has half-rectified the (a.c. power) supply

1

[12]