

**Name of the Student:** \_\_\_\_\_

**Max. Marks : 17 Marks**

**Time : 17 Minutes**

**Q1.**

- (a) Describe the difference between an alternating current (a.c.) and a direct current (d.c.).

---


---

---

---

(2)

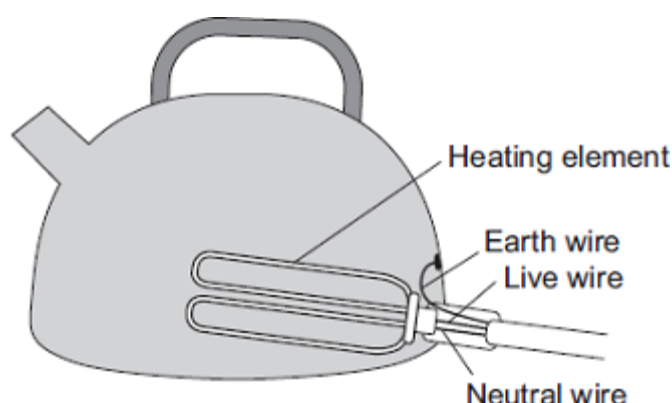- (b) The diagram shows how the electric supply cable is connected to an electric kettle. The earth wire is connected to the metal case of the kettle.



If a fault makes the metal case live, the earth wire and the fuse inside the plug protect anyone using the kettle from an electric shock.

Explain how.

---

---

---

---

(2)

**(Total 4 marks)**

**Q2.**

The table gives data about two types of low energy bulb.

Type of bulb	Power input in watts	Efficiency	Lifetime in hours	Cost of one bulb
Compact Fluorescent Lamp (CFL)	8	20%	10 000	£3.10
Light Emitting Diode (LED)	5		50 000	£29.85

(a) Both types of bulb produce the same useful power output.

(i) Calculate the useful power output of the CFL.

Show clearly how you work out your answer.

---



---



---

Useful power output = \_\_\_\_\_ W

(2)

(ii) Calculate the efficiency of the LED bulb.

Show clearly how you work out your answer.

---



---



---

Efficiency = \_\_\_\_\_

(1)

(b) LED bulbs are expensive. This is because of the large number of individual electronic LED chips needed to produce sufficient light from each bulb.

(i) Use the data in the table to evaluate the cost-effectiveness of an LED bulb compared to a CFL.

---



---



---



---

(2)

(ii) Scientists are developing brighter and more efficient LED chips than those currently used in LED bulbs.

Suggest **one** benefit of developing brighter and more efficient LED chips.

---

**Q3.**

- (a) The resistance of a 24 W, 12 V filament lamp depends on the current flowing through the lamp. For currents up to 0.8 A, the resistance has a constant value of 2.5  $\Omega$ .

- (i) Use the equation in the box to calculate the potential difference across the lamp when a current of 0.8 A flows through the lamp.

$$\text{potential difference} = \text{current} \times \text{resistance}$$

Show clearly how you work out your answer.

---


---

Potential difference = \_\_\_\_\_ V

(2)

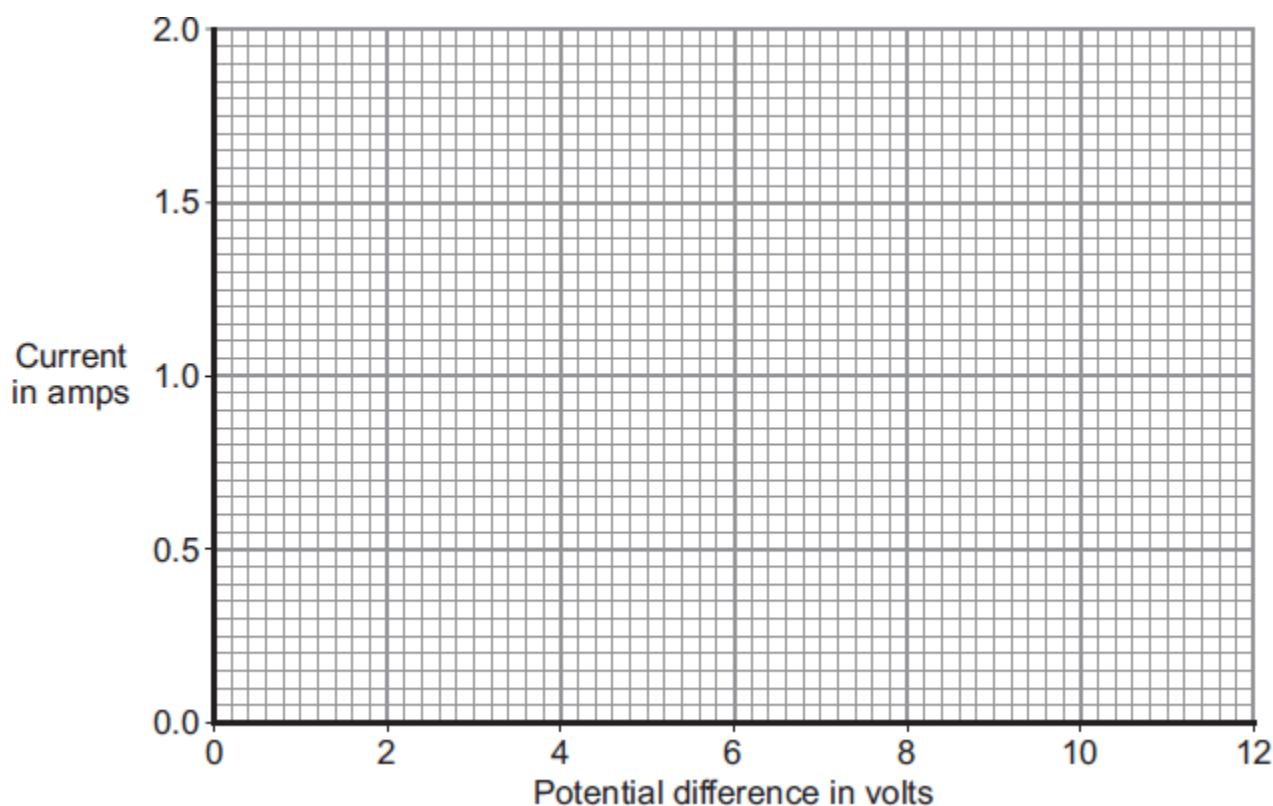- (ii) When the potential difference across the lamp is 12 V, the current through the lamp is 2 A.

On the axes below, draw a current–potential difference graph for the filament lamp over the range of potential difference from 0 to 12 volts.




(2)

- (iii) Why does the resistance of the lamp change when the current through the lamp exceeds 0.8 A?

(1)

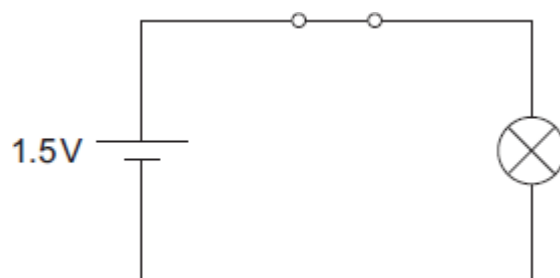- (b) The lamp is now included in a circuit. The circuit is switched on for 2 minutes. During this time, 72 coulombs of charge pass through the lamp.



Use the equation in the box to calculate the energy transformed by the lamp while the circuit is switched on.

$\text{energy transformed} = \text{potential difference} \times \text{charge}$
--

Show clearly how you work out your answer.

Energy transformed = \_\_\_\_\_ J

(2)

(Total 7 marks)