


Name of the Student: _____

Max. Marks : 10 Marks

Time : 10 Minutes

Q1.

- (a) The picture shows a new washing machine.

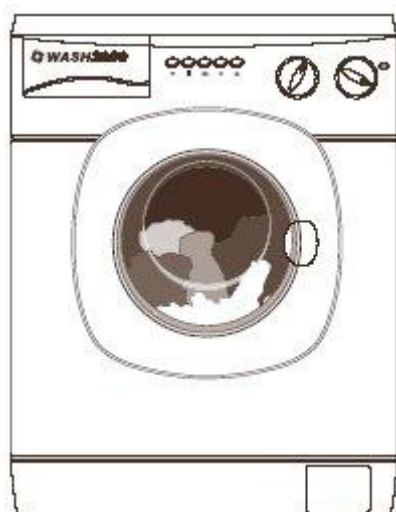Complete the following sentence using **one** of the words in the box.**kinetic****light****sound**

A washing machine is designed to transform electrical energy into heat and

_____ energy

(1)

- (b) The instruction booklet for the washing machine contains the following information.

Wash cycle	Average power during cycle	Time taken to run cycle
HOT	1.5 kW	2 hours
COOL	1.1 kW	1½ hours
FAST	1.0 kW	¾ hour

- (i) Use the following equation to calculate the energy transferred, in kilowatt-hours, to the washing machine during the HOT wash cycle. Show how you work out your answer.

$$\text{energy transferred} = \text{power} \times \text{time}$$

Energy transferred = _____ kWh

(2)

- (ii) Why does it cost more to use the washing machine on the HOT cycle than on the COOL or FAST cycle?

(1)

- (iii) Before buying a washing machine, a householder researched several makes to find out which washing machine was the most energy efficient.


Write down **one** way that he could have done this research.

(1)

(Total 5 marks)

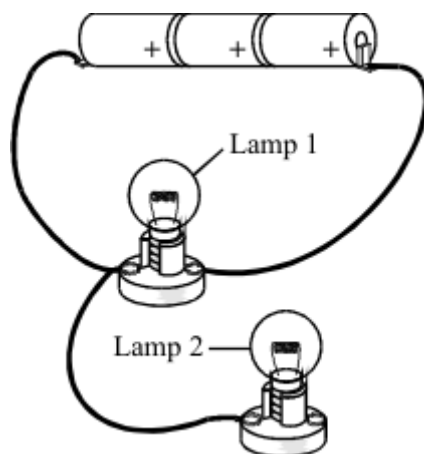Q2.

The drawing shows three identical cells and two identical lamps joined in a circuit.



- (a) Use the correct symbols to draw a circuit diagram for this circuit.

(3)

- (b) Each of the cells provides a potential difference (voltage) of 1.5 volts. What is the total potential difference (voltage) provided by all three cells?

_____ volts

(1)

- (c) Complete this sentence by crossing out the **two** lines in the box that are wrong.

smaller than
the same as
bigger than

The current through lamp 2 will be _____ the current through lamp 1.

(1)

(Total 5 marks)