

Name of the Student: \_\_\_\_\_

Max. Marks : 23 Marks

Time : 23 Minutes

Mark Schemes

**Q1.**

(a)  $97\,500 = 65.0 \times t$

1

$$t = \frac{97500}{65.0}$$

1

$t = 1500 \text{ (s)}$

*an answer of 1500 (s) scores 3 marks**an answer of 1.5 scores 2 marks*

1

(b)  $19.6 = I^2 \times 1.60$

1

$$I^2 = \frac{19.6}{1.60}$$

1

$I = 3.5 \text{ (A)}$

*allow 1 mark for a correct value for I correctly multiplied by 4*

1

current through battery = 14 (A)

*an answer of 14 (A) scores 4 marks*

1

**[7]****Q2.**

(a) negatively charged

1

electrons are transferred

1

from the (neutral) object

1

(b) minimum of four lines drawn perpendicular to surface of sphere  
*judge by eye*

1

minimum of one arrow shown pointing away from sphere  
*do **not** accept any arrow pointing inwards.*

(c) Q


1

1

[6]

Q3.

(a)

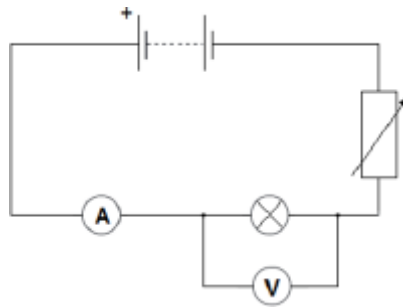

*battery in series with bulb and ammeter*

1

*voltmeter in parallel with bulb*

1

*variable resistor*

**or**

*variable power pack*

**or**

*potentiometer*

1

(b) A is brighter because it has a higher current (than lamp B at any p.d.)

1

(therefore A has a) higher power output (than bulb B)

*accept higher energy output per second*

1

(c) lower current (than lamp A) for the same potential difference

*accept answer in terms of  $R = V / I$*

*allow reference to a comparison of the gradients*

1

this is true for all values (of p.d. on the graph)

1

(d) 0 – 2 Volts

*allow a range from 0 V up to any value between 1 and 2 V.*

1

(for an ohmic conductor) current is directly proportional to potential difference

*allow lines (of best fit) are straight and pass through the origin*

1

(so) resistance is constant

1

[10]