


Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

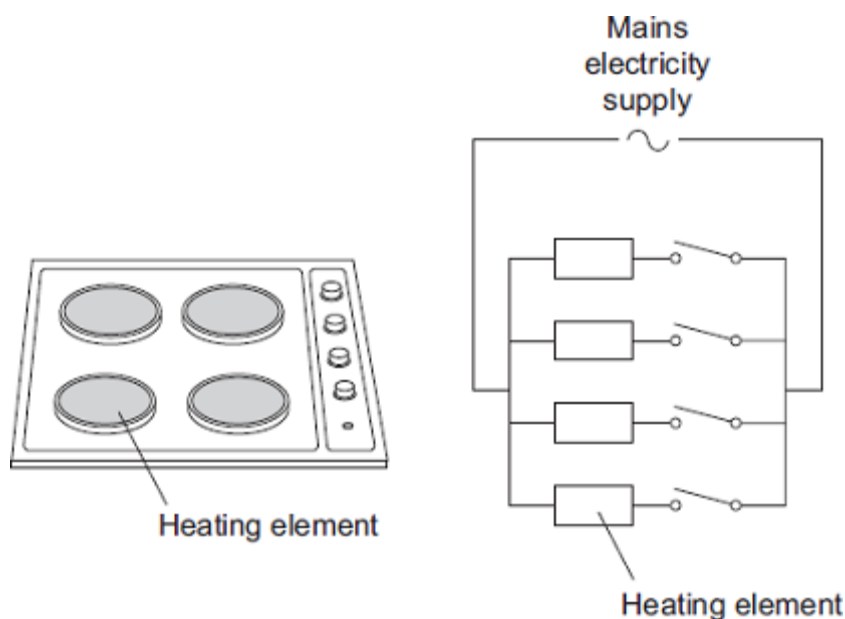Q1.

The picture shows an electric cooker hob. The simplified circuit diagram shows how the four heating elements connect to the mains electricity supply. The heating elements are identical.



When all four heating elements are switched on at full power the hob draws a current of 26 A from the 230 V mains electricity supply.

- (a) Calculate the resistance of one heating element when the hob is switched on at full power.

Give your answer to 2 significant figures.

Resistance = _____ Ω **(3)**

- (b) The table gives the maximum current that can safely pass through copper wires of different cross-sectional area.

Cross-sectional area in mm ²	Maximum safe current in amps

1.0	11.5
2.5	20.0
4.0	27.0
6.0	34.0

The power sockets in a home are wired to the mains electricity supply using cables containing 2.5 mm^2 copper wires. Most electrical appliances are connected to the mains electricity supply by plugging them into a standard power socket.

It would **not** be safe to connect the electric cooker hob to the mains electricity supply by plugging it into a standard power socket.

Why?

(2)

- (c) Mains electricity is an alternating current supply. Batteries supply a direct current.


What is the difference between an alternating current and a direct current?

(2)



(Total 7 marks)

Q2.

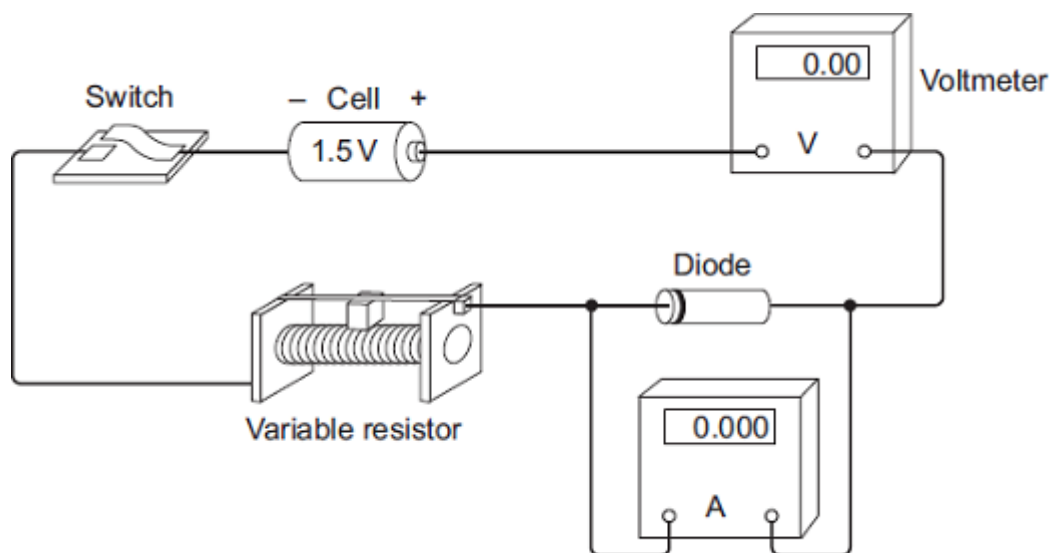- (a) A student set up the circuit shown in the diagram. The student uses the circuit to obtain the data needed to plot a current - potential difference graph for a diode.



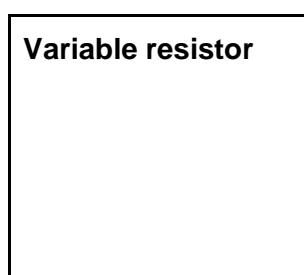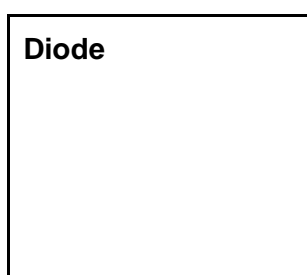- (i) Draw, in the boxes, the circuit symbol for a diode and the circuit symbol for a variable resistor.



(2)

- (ii) The student made two mistakes when setting up the circuit.


What **two** mistakes did the student make?

1. _____

2. _____

(2)

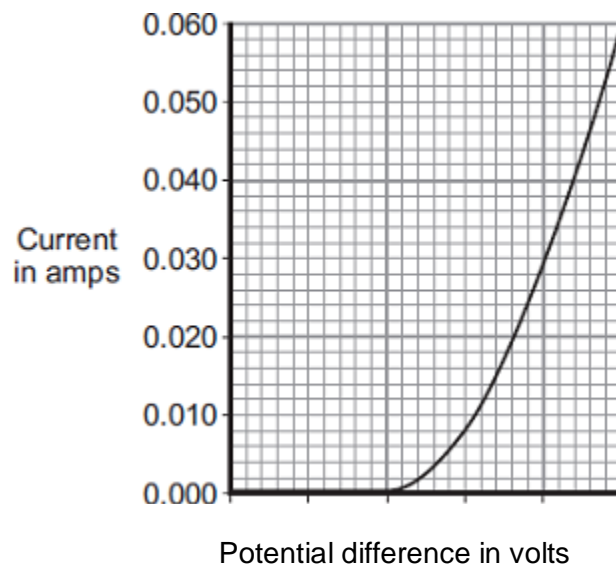- (b) After correcting the circuit, the student obtained a set of data and plotted the graph below.



- (i) At what potential difference did the diode start to conduct an electric current?

_____ V


(1)

- (ii) Use data from the graph to calculate the resistance of the diode when the potential difference across the diode is 0.3 V.

Resistance = _____ ohms

(3)

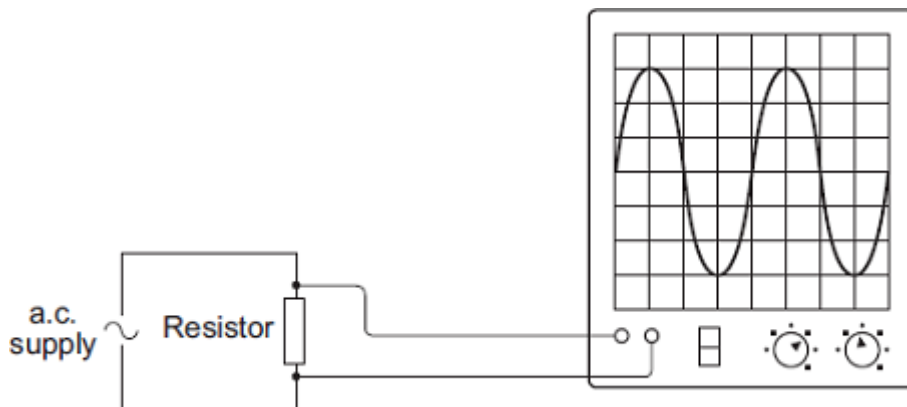- (c) The diagram shows the trace produced by an alternating current (a.c.) supply on an oscilloscope.




Each horizontal division on the oscilloscope screen represents a time of 0.01s.

- (i) Calculate the frequency of the a.c. supply.

Frequency = _____ hertz

(2)

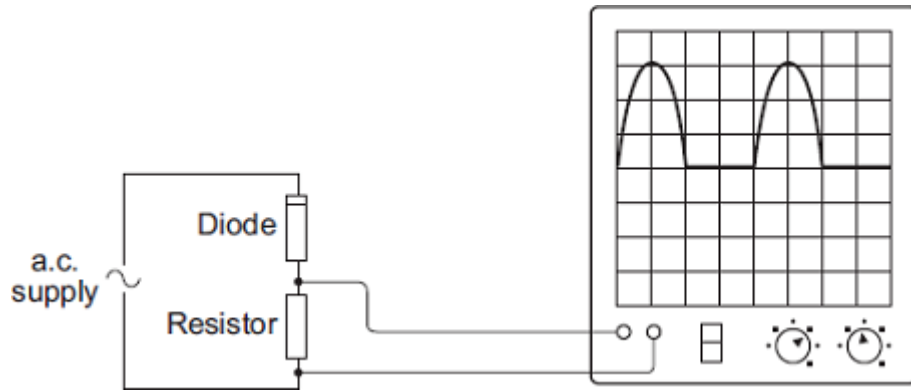- (ii) A diode is now connected in series with the a.c. power supply.



Why does the diode cause the trace on the oscilloscope screen to change?

(2)

(Total 12 marks)