

Name of the Student: _____

Max. Marks : 18 Marks

Time : 18 Minutes

Mark Schemes

Q1.

(a) (i) $P = V \times I$

or equivalent

*credit a triangle if part (ii) correctly uses the relationship**credit power = volts \times amps or watts $V \times A$* *do not accept C for current*

1

(ii) $(P = 230 \times 10 =) 2300$

credit 2.3

1

W or J/s

kW

1

(b) (i) 15 A

credit 13 A or amps

1

(ii) any **three** from

earth

any short (to the metal tank) causes fuse to blow

fuse is in the live wire

to prevent damage to the heater

credit to stop the current

3

(c) (i) $V = I \times R$

or equivalent

credit a triangle if part (ii) correctly uses the relationship

1

(ii) $(230 = 10 \times R =) 23$

ohms or Ω

2

[10]

Q2.

- (a) *Formula mark*

$$P = V \times I$$

*accept $P = VI$ **or** $W = V 5 A$ **or** any transformation*

1

Substitution mark $I = 900 \div 230$

1

Calculation mark 3.9

*accept 3.9 **or** 3.91 **or** 4 for three marks with no working*

1

- (b) $900 + 1300 = 2200 \div 230 = 9.6$

*accept 9.57 to 9.6 **or** 10 for both marks with no working*

2

- (c) $1.2 + 0.45 = 1.65$

1

$$\times 0.5 = 0.825$$

*accept 0.8 **or** 0.83 for both marks with no working*

1

- (d) any **one** from

use less energy (to cook something)

*accept fewer energy losses **or** use less electricity*

cook faster

do not credit a cost argument about buying two different ovens

1

[8]