

Name of the Student: _____


Max. Marks : 17 Marks

Time : 17 Minutes

Q1.

Figure 1 shows a circuit diagram.

Figure 1

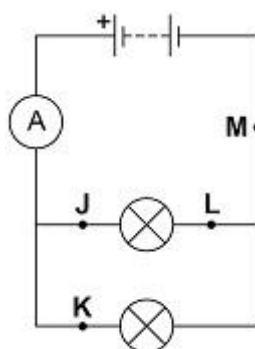

- (a) In which position could a switch be placed so that both lamps can be switched on or off at the same time?

Tick (✓) **one** box.

J	<input type="checkbox"/>	K	<input type="checkbox"/>	L	<input type="checkbox"/>	M	<input type="checkbox"/>
---	--------------------------	---	--------------------------	---	--------------------------	---	--------------------------

(1)

- (b) Draw the circuit symbol for a switch in the box below.

(1)

- (c) In 30 seconds, 24 coulombs of charge flow through the battery.

Calculate the current in the battery.

Use the equation:

$$\text{current} = \frac{\text{charge flow}}{\text{time}}$$

Current = _____ A

(2)

- (d) There is a potential difference of 3.6 V across the battery.

Calculate the energy transferred by the battery when 60 coulombs of charge flows through the battery.

Use the equation:

$$\text{energy transferred} = \text{charge flow} \times \text{potential difference}$$


Energy transferred = _____ J

(2)

A student built **Circuit X** and **Circuit Y** shown in **Figure 2**.

The components used in each circuit were identical.

Figure 2

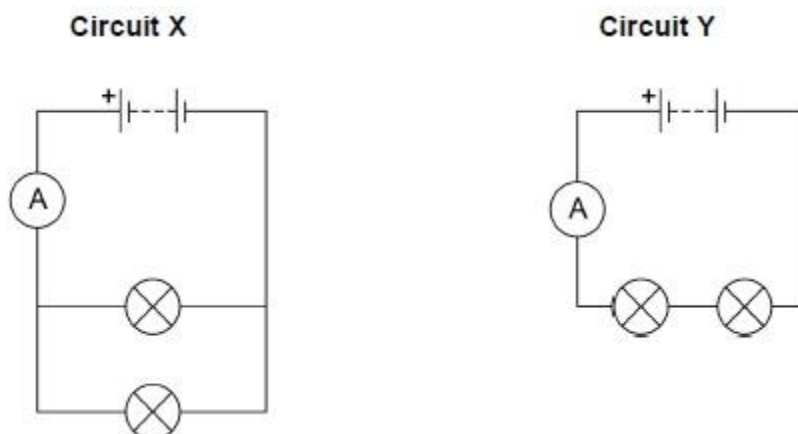

- (e) How would the reading on the ammeter in **Circuit Y** compare to the reading on the ammeter in Circuit X?

Tick (✓) **one** box.

The reading in **Y** would be higher.

☐

The reading in **Y** would be lower.

☐

The readings would be the same.

☐

(1)

- (f) How does the total resistance of **Circuit Y** compare with the total resistance of **Circuit X**?

Tick (✓) **one** box.

The total resistance of **Y** is greater.

☐

The total resistance of **Y** is less.

☐


The total resistance is the same.

☐

(1)

The student built another circuit which is shown in **Figure 3**.

Figure 3

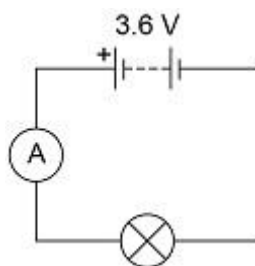

- (g) Write down the equation which links current, potential difference and resistance.

(1)

- (h) There is a potential difference of 3.6 V across the lamp in **Figure 3**.

The current through the lamp is 0.80 A


Calculate the resistance of the lamp.

Resistance = _____ Ω

(3)

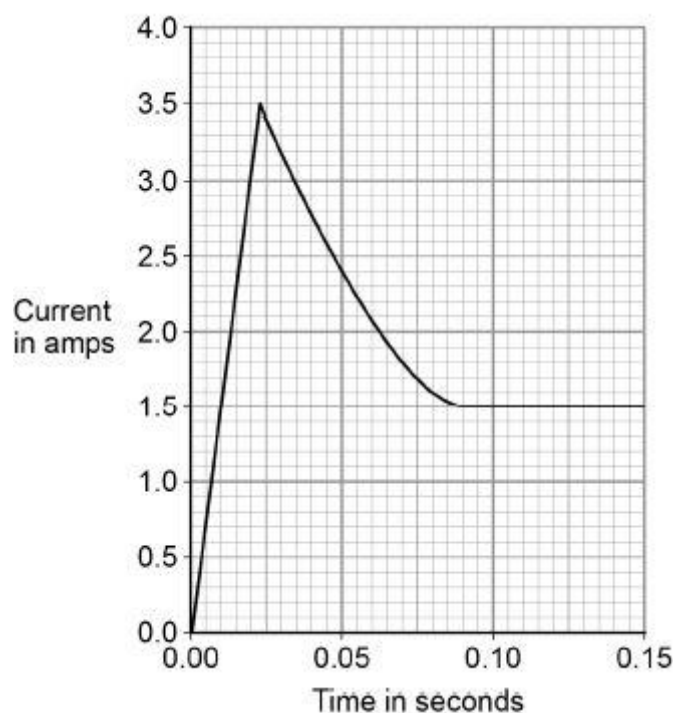Q2.

The graph below shows how the current through a filament lamp changes after the lamp is switched on.



- (a) The normal current through the filament lamp is 1.5 A.

For how many seconds is the current through the filament lamp greater than 1.5 A?

Tick **one** box.

0.01 s

☐

0.08 s

☐

0.09 s

☐

0.14 s

☐

(1)

- (b) Why might the filament inside a lamp melt when the lamp is first switched on?

(1)

- (c) The lamp is connected to a 24 V power supply. The current through the lamp is 1.5 A.

Calculate the power of the lamp.

Use the equation:

$$\text{power} = \text{potential difference} \times \text{current}$$

Power = _____ W

(2)

- (d) LED lamps are much more efficient than filament lamps.

What does this statement mean?

Tick **one** box.

LED lamps have a similar power output to filament lamps.

☐

LED lamps waste a smaller proportion of the input energy than filament lamps.

☐

LED lamps have a higher power input than filament lamps.

☐

LED lamps waste a larger proportion of the input energy than filament lamps.

☐

(1)

(Total 5 marks)