

Name of the Student: _____

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

Q1.

- | | | |
|-----|---|---|
| (a) | 20 | 1 |
| (b) | 50 | 1 |
| (c) | (i) 115 | 1 |
| | (ii) 230 | 1 |
| | (iii) if one goes out the other still works
or
brighter
<i>accept power (output) is greater</i>
<i>can be switched on/off independently is insufficient</i> | 1 |
| (d) | the outside/casing is plastic
<i>there is plastic around the wires is insufficient</i>
<i>it is plastic is insufficient</i> | 1 |
| | and plastic is an insulator
<i>an answer the light fitting is double insulated gains both marks</i> | 1 |
| (e) | (residual current) circuit breaker
<i>accept RCCB</i>
<i>accept RCBO</i>
<i>accept RCCD</i>
<i>accept RCB</i>
<i>accept miniature circuit breaker / MCB</i>
<i>trip switch is insufficient</i>
<i>breaker is insufficient</i>
<i>do not accept earth wire</i> | 1 |

[8]

Q2.

(a) 4

1

(b) (i) 2

allow 1 mark for correct substitution ie

$$I = \frac{100}{20}$$

provided no subsequent step

2

(ii) 5

allow 1 mark for correct substitution ie

$$V = \frac{100}{20}$$

provided no subsequent step

2

[5]**Q3.**

(a) last box ticked



1

(b) (i) use hotter water (than 60 °C)

*accept use boiling water**accept use water at any stated temperature above 60 °C***or**

add ice cubes

*accept add water at any stated temperature below 12 °C**use different temperatures is insufficient*

1

(ii) the current increases as the temperature increases

1

(iii) 0.02 (A)

1

(iv) 5 (V)

ortheir **(b)(iii)** × 250 correctly calculated*allow 1 mark for correct substitution ie $V = 0.02 \times 250$* **or** *$V = \text{their } \mathbf{(b)(iii)} \times 250$*

2

(v) the resistance increases

1

[7]