

Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

Mark Schemes

Q1.

(a) (i) A 1

(ii) bar drawn with correct height
 ignore width of bar 1

(b) (i) $E = P \times t$
 2.4
 allow 1 mark for correct substitution
 ie 1.2×2
 provided no subsequent step shown 2

(ii) 36 or their (b)(i) $\times 15$ correctly calculated
 or
 their (b)(i) $\times 0.15$ correctly calculated with an answer given in £
 allow 1 mark for correct substitution
 ie 2.4×15
 or
 their (b)(i) $\times 15$
 allow 1 mark for correct substitution
 provided no subsequent step shown
 an answer £0.36 gains both marks 2

[6]**Q2.**

(a) (i) 15 1

(ii) 4.5 or their (a)(i) $\times 0.3$ correctly calculated
 allow 1 mark for correct substitution, ie 0.3×15 /their (a)(i), provided no
 subsequent step 2

(ii) decrease 1

(b) Y

accept any correct indication
reason only scores if Y is chosen
accept voltage for p.d.

1

(only one that) shows a direct current / p.d.

or

a battery / cell gives a direct current

accept both X and Z are a.c.

or

a battery/cell gives a constant current/p.d.

accept it's a constant current/p.d.


it is not changing is insufficient

1

[6]

Q3.

(a) (i) correct symbol ringed

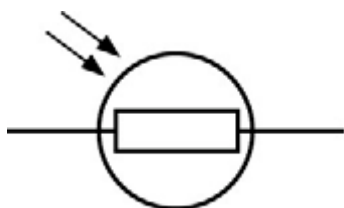

1

(ii) accept any suggestion that would change light intensity, eg:

- torch on or off
accept power of torch
*do **not** accept watts / wattage of torch*
- distance between torch and LDR
- lights in room on or off
- shadow over the LDR

1

(b) resistance decreases

1

from 600 k Ω to 200 k Ω

accept by 400 k Ω

1

(c) (i) no numbers for light intensity

or

light intensity is categoric / a description / not continuous

not enough results is insufficient

1

(ii) YES

mark is for the reason

both show that resistance increases with decreasing (light)
intensity / brightness

accept they both get the same results / pattern

1

- (d) A circuit that automatically switches outside lights on when it gets dark.

1

[7]