


Name of the Student: \_\_\_\_\_

Max. Marks : 18 Marks

Time : 18 Minutes

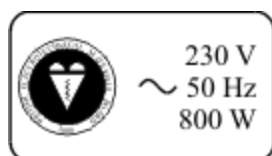**Q1.**

The information plate on a hairdrier is shown.



- (a) What is the power rating of the hairdrier?

\_\_\_\_\_

(1)

- (b) (i) Write down the equation which links current, power and voltage.

\_\_\_\_\_

(1)

- (ii) Calculate the current in amperes, when the hairdrier is being used. Show clearly how you work out your answer.

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Current = \_\_\_\_\_ amperes


(2)

- (iii) Which **one** of the following fuses, 3A, 5A or 13A, should you use with this hairdrier?

\_\_\_\_\_

(1)

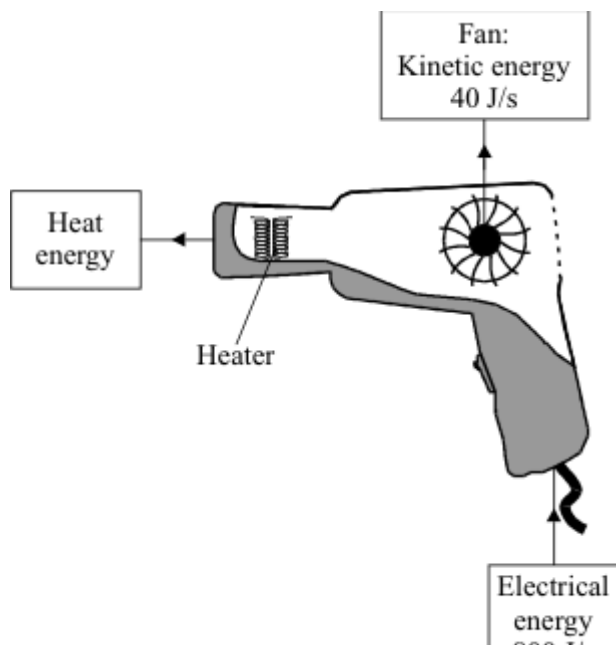- (c) The hairdrier transfers electrical energy to heat energy and kinetic energy.



Calculate the efficiency of the hairdrier in transferring electrical energy into heat energy.

---



---



---


Efficiency = \_\_\_\_\_

(2)


(Total 7 marks)

## Q2.

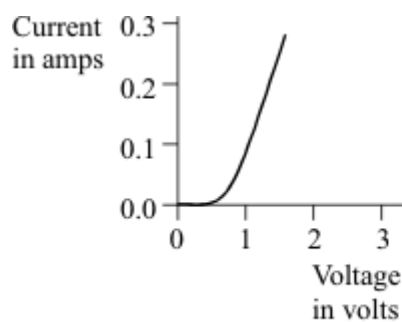
(a) The diagram shows the voltage-current graphs for three different electrical components.



A

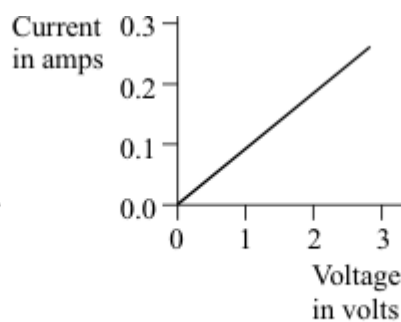

B

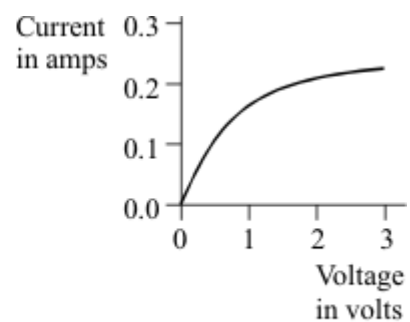

C

Which **one** of the components **A**, **B** or **C** could be a 3 volt filament lamp? Explain the reason for your choice.

---



---




---



---

(3)

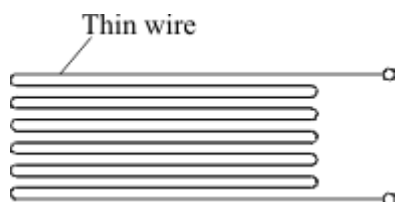- (b) Using the correct symbols draw a circuit diagram to show how a battery, ammeter and voltmeter can be used to find the resistance of the wire shown.



(3)

- (c) When correctly connected to a 9 volt battery the wire has a current of 0.30 amperes flowing through it.

- (i) Give the equation that links current, resistance and voltage.

\_\_\_\_\_

(1)

- (ii) Calculate the resistance of the wire. Show clearly how you work out your answer and give the unit.

\_\_\_\_\_

\_\_\_\_\_

Resistance = \_\_\_\_\_

(3)

- (iii) When the wire is heated, the current goes down to 0.26 amperes. State how the resistance of the wire has changed.

\_\_\_\_\_

\_\_\_\_\_

(1)

(Total 11 marks)