


Name of the Student: _____

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

Q1.

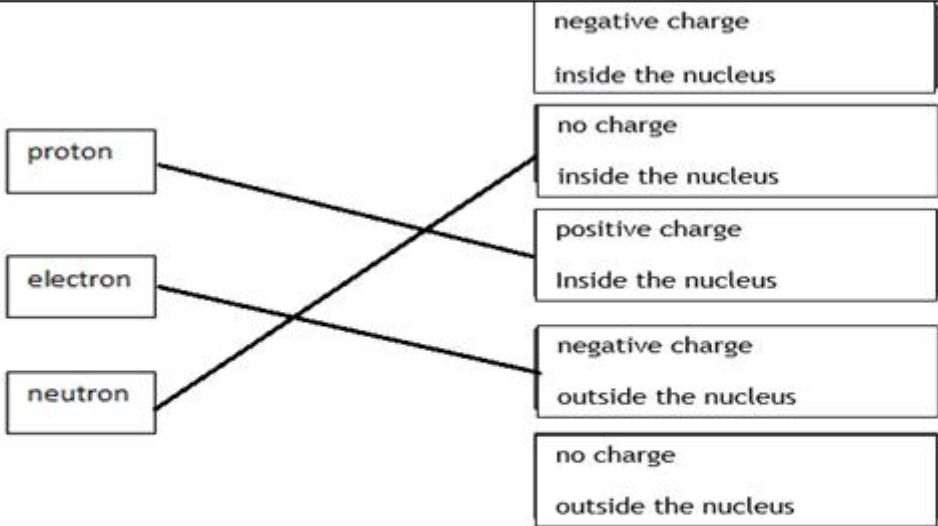Question Number	Answer	Mark
	 <p>One mark for each correct line.</p> <p>More than one line from a box on the left loses the mark for that box.</p>	(3)

Q2.

Question number	Answer	Mark
	1.4 (A)	(1) AO2

Q3.

Question number	Answer	Additional guidance	Mark
	<p>an explanation linking any three from:</p> <p>lamp in second circuit is dimmer (than lamp in first circuit) (1)</p> <p>current in second circuit is less (than in first circuit) (1)</p> <p>potential difference / voltage across each lamp (in second circuit is) less / shared (1)</p> <p>idea that power of each lamp (in second circuit) is less / shared (1)</p> <p>the (total) resistance of the second circuit is more (than in first circuit) (1)</p>	<p>accept reverse arguments throughout</p>	<p>(3)</p> <p>A01</p>

Q4.

Question number	Answer	Mark
(i)	either power = (current) ² × resistance or $P = I^2 \times R$	(1)

Question number	Answer	Additional guidance	Mark
(ii)	substitution into $P = I^2 \times R$ (1) $55 = 4.4^2 \times R$ rearrangement (1) $R = P \div I^2$ evaluation (1) $2.8 (\Omega)$	Substitution and re-arrangement in either order $R = 55 \div 4.4^2$ for 2 marks allow answers that round to 2.8 award full marks for correct answer without working allow alternative route $V = P \div I = 55 \div 4.4$ then $R = V \div I = 12.5 \div 4.4$	(3)

Question number	Answer	Additional guidance	Mark
(i)	0.9 (v)	0.90 ignore units ignore calculations	(1)

Question number	Answer	Additional guidance	Mark
(ii)	substitution (1) $R = \frac{2.1}{0.041}$ evaluation (1) $R = 51(.2) (\Omega)$ (which is approx. 50 (Ω))	allow $(V) = 0.041 \times 50$ $V = 2.05 (v)$ (which is approx. 2.1) allow $R = 51(.2) (\Omega)$ with no working for 2 marks	(2)

Question number	Answer	Additional guidance	Mark
(iii)	recall and substitution (1) $(P) = 2.1 \times 0.041$ evaluation (1) $(P =) 0.086 (W)$	 allow any value that rounds to 0.086; e.g. 0.0861 (W) 0.09 (W) award full marks for the correct answer without working allow POT error for 1 mark	(2)

Question number	Answer	Additional guidance	Mark
(iv)	<p>recall that effective resistance = sum of individual resistances (1)</p> <p>(resistance =) $50 + 22$</p> <p>evaluation (1)</p> <p>$72 (\Omega)$</p>	<p>$51 + 22$</p> <p>$73 (\Omega)$</p> <p>award full marks for the correct answer without working</p>	(2)

Question number	Answer	Additional guidance	Mark
(v)	<p>substitution (1)</p> <p>(E =) $3.0 \times 0.041 \times 2 \times 60$</p> <p>evaluation (1)</p> <p>15 (J)</p>	<p>accept values that round to 15; e.g. 14.76</p> <p>award full marks for the correct answer without working</p> <p>award 1 mark for answer of 0.246 (J) or 0.25 (J) without working</p>	(2)